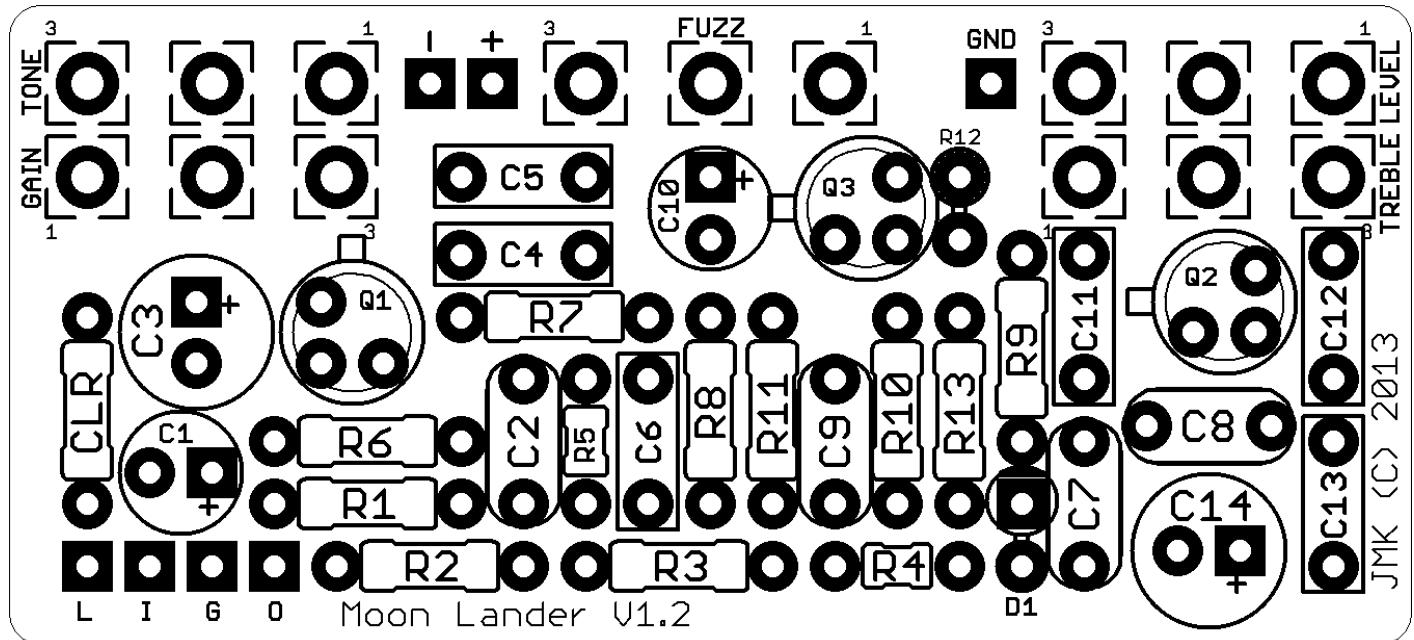


JMK PCBs PRESENTS...


MOON LANDER

PCB AND SCHEMATIC ARTWORK (C) 2014 JMK PEDALS
VERSION 1.2.1: 10/1/2014



| Resistors | | | | Capacitors | | | | Transistors | |
|-----------|------|-----|------|------------|--------|-----|--------|------------------------|--------|
| R1 | 56K | R8 | 100R | C1 | 10uF* | C8 | 220pF | Q1-Q3 | BC109 |
| R2 | 100K | R9 | 100K | C2 | 100pF | C9 | 220pF | Diodes | |
| R3 | 470K | R10 | 56K | C3 | 100uF* | C10 | 100uF* | D1 | 1N4001 |
| R4 | 100R | R11 | 56K | C4 | 5.6nF | C11 | 15nF | Potentiometers | |
| R5 | 10K | R12 | 10K | C5 | 220nF | C12 | 3.3nF | LEVEL, TREBLE, TONE | A100K |
| R6 | 100R | R13 | 2.7K | C6 | 4.7nF | C13 | 2nF | FUZZ | B1K |
| R7 | 820R | CLR | 4.7K | C7 | 470pF | C14 | 100uF* | GAIN | B2K |

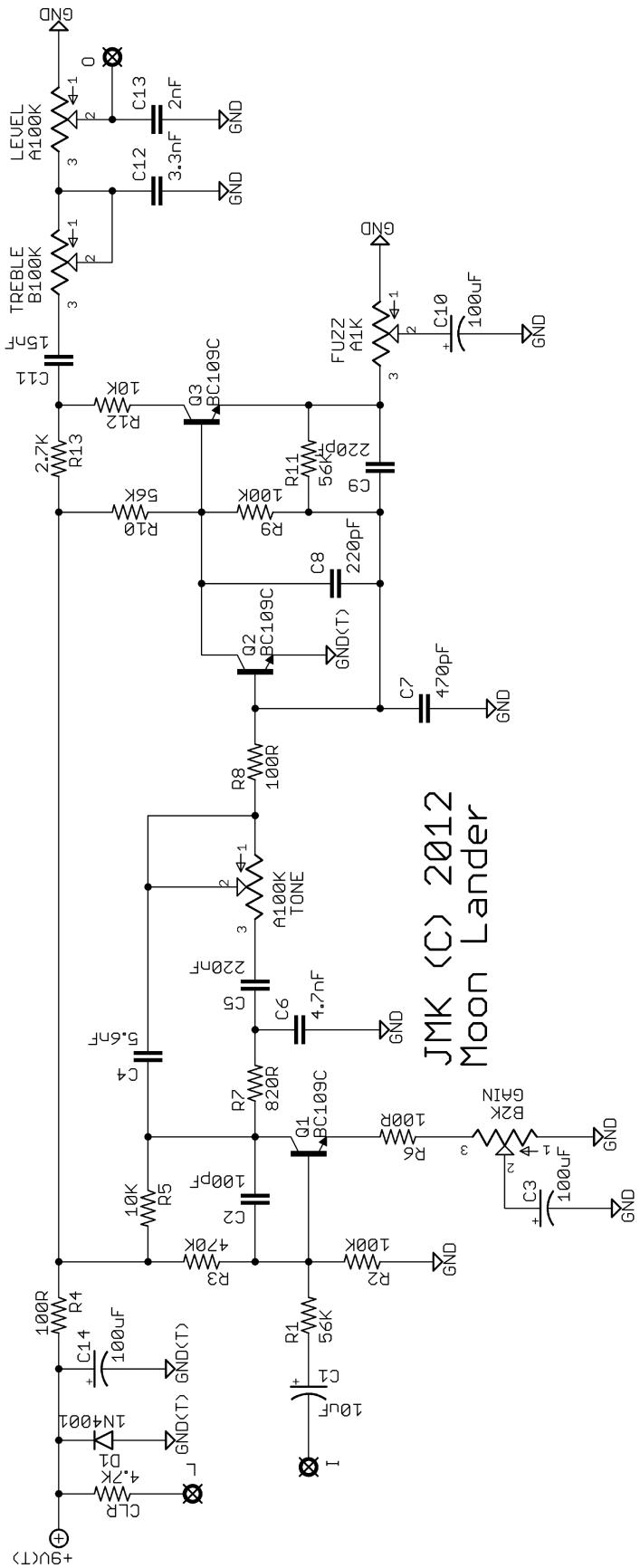This Document is designed for personal use only! Do not use this to create a product for sale without permission of it's owner: jmkpcbs@gmail.com



This Document is designed for personal use only! Do not use this to create a product for sale without permission of it's owner: jmkpcbs@gmail.com

BUILD NOTES

- The Moon Lander is a slightly modified clone of the Lunar Deluxe circuit, which is in turn based on a silicon transistor based Fuzz Face. This version features small modifications to the original, but is generally the same in the core of the circuit. This circuit is generally thought of as a very versatile for both fuzz and overdrive tones.
- Hooking up the PCB is pretty simple, but to clarify: L = the connection for the + end of an LED (CLR is marked on the board); I = PCB Input; G = Ground for the Switch; O = PCB Output; + = 9V input; - = Ground for DC Jack; GND = Extra Ground for a 1/4" Jack
- Like with most Fuzz Pedals, the Transistors are an integral part of the sound. Pretty much any NPN BiPolar transistor can be used. Keep in mind that the pinout of the transistor needs to be considered when installing. **We highly recommend socketing your transistors!** Socketing allows you to switch your transistors easily if you have installed them backwards, and also allows you to swap out and try other transistors to see which you like the best. Options to try include, but is not limited to: BC108, 2N5088, 2N5089, 2N3904, BC549, BC550, and BC560. Don't forget to check your pinouts to make sure they match up with the BC109 specified in the Schematic.

TRUE BYPASS WIRING DIAGRAM

EFFECT INPUT LED- EFFECT OUTPUT

