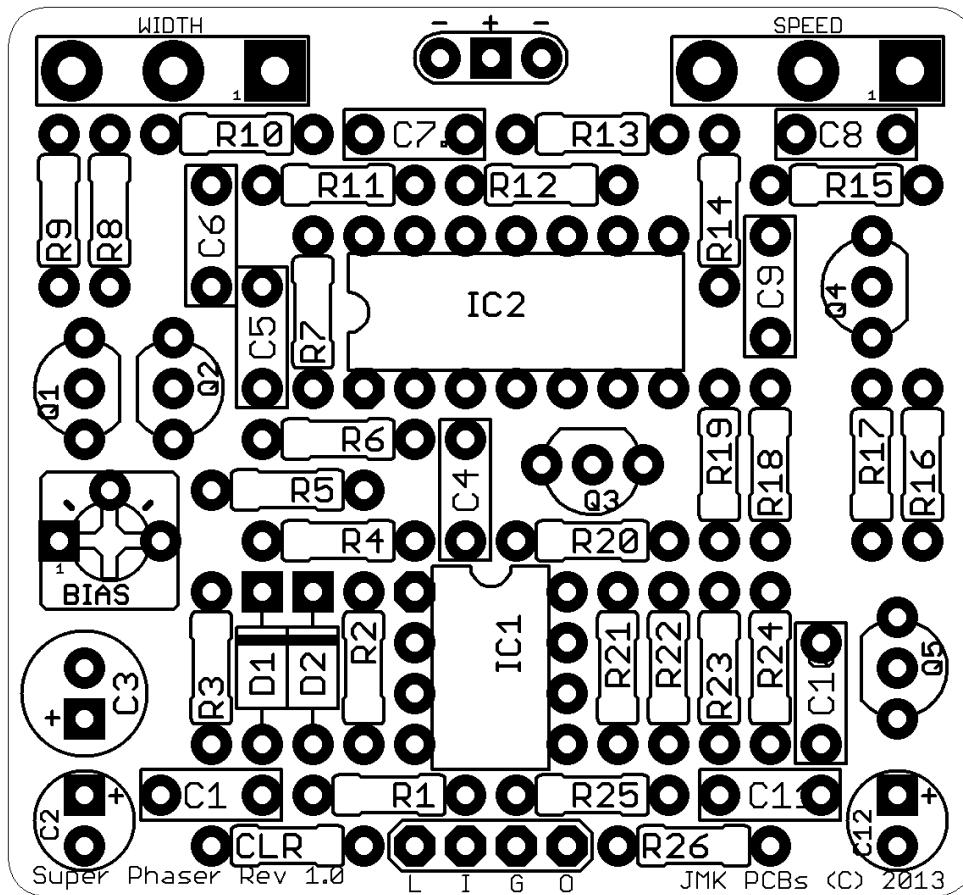


JMK PCBs PRESENTS...


THE SUPER PHASER

PCB AND SCHEMATIC ARTWORK (C) 2014 JMK PEDALS
VERSION 1.0.2: 10/22/2014



Resistors						Capacitors				Semiconductors	
R1	10K	R10	10K	R19	150K	C1	10nF	C7	47nF	Q1-Q4	2N5952
R2	10K	R11	10K	R20	150K	C2	10uF	C8	100nF	Q5	2N5087
R3	470K	R12	22K	R21	150K	C3	100uF	C9	47nF	IC1	Dual Op Amp
R4	10K	R13	10K	R22	470K	C4	47nF	C10	10nF	IC2	Quad Op Amp
R5	22K	R14	10K	R23	150K	C5	47nF	C11	47nF	Potentiometer	
R6	10K	R15	22K	R24	150K	C6	47nF	C12	15uF	WIDTH	B1M
R7	10K	R16	4.6K	R25	56K	Diodes				SPEED	C500K
R8	22K	R17	3.9M	R26	150K	D1	5.1V Zener			BIAS	250K
R9	22K*	R18	10K	CLR	4.7K	D2	1N4001				

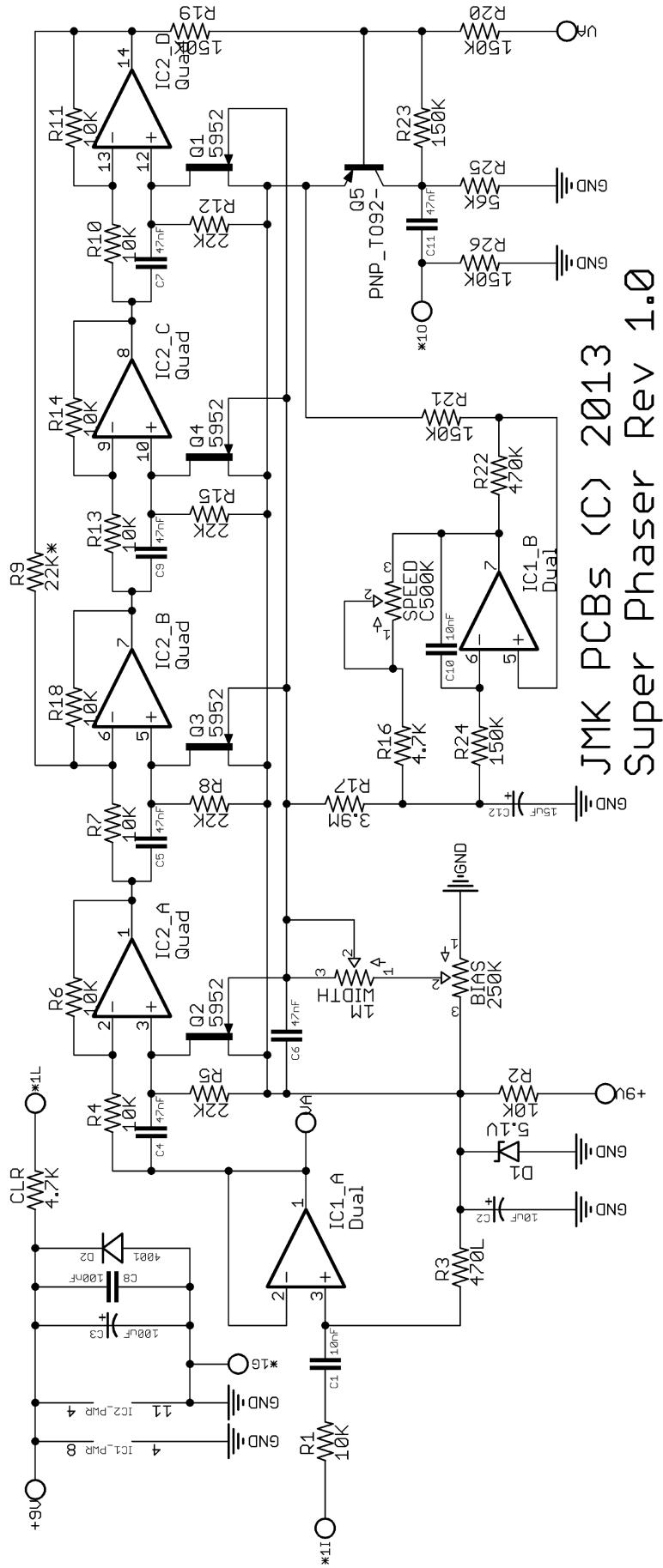This Document is designed for personal use only! Do not use this to create a product for sale without permission of it's owner: jmkpcbs@gmail.com



This Document is designed for personal use only! Do not use this to create a product for sale without permission of it's owner: jmkpcbs@gmail.com

BUILD NOTES

- The Super Phaser is basically a simple 4 stage JFet phaser. These phasers have been very popular for a very long time, and with the addition of the mods we have included, it becomes slightly more ‘tunable’ for the average user.
- The Super Phaser’s core is based around 4 JFet transistors. Please note that JFets are generally out of production now, and in particular, the 2N5952 type that are most common for this build are getting harder and harder to find. There are SMD types available out there if you want to go that route, however, you can still (as of the writing of this doc) reliably get JFet transistors from Smallbear Electronics in small amounts.
- The 4 JFet transistors in this build are integral to the quality of the phase sounds the user will get. In particular, the 4 transistors should be matched. This means that the negative vgs rating of each transistor is either identical or very close to each other. For more information on matching, you can certainly find lots of info by Googling the subject, or you can also take a look at [this](#) DIY project from JMK PCBs.
- The modification applied to this circuit is very simple: A width control. We call it a width control because it acts more like a width adjustment to the phase signal than a depth control. Essentially, it replaces a 1M resistor with a variable resistor via the potentiometer. In conjunction with the Speed pot, there is a lot more flexibility in the Phase sound available from this pedal.
- Hooking up the PCB is pretty simple, but to clarify: L = the connection for the + end of an LED (CLR is marked); I = PCB Input; G = Ground for the Switch; O = PCB Output; + = 9V input; - = Ground for DC Jack; - = Extra Ground for 1/4” Jack
- **We highly recommend socketing your transistors and ICs!** Socketing allows you to switch your semiconductors easily if you have installed them backwards, and also allows you to swap out and try other transistors to see which you like the best. Consider the parts you use carefully, and check pinouts for replacements against the datasheets for each of the parts we’ve recommended.

TRUE BYPASS WIRING DIAGRAM

EFFECT INPUT LED- EFFECT OUTPUT

