

Description:

Welcome to the Dark Side. The Superjudge is a distortion circuit created by Juansolo and Cleggy (famous from the www.madbeanpedals.com forum) and is a very easy-to-build distortion. The basis of the Superjudge starts with an 18v charge pump on board which boosts the voltage from 9v to 18v. Add two inverting opamp stages, combined with a LED clipping stage, and wrap it up with a tone control. This distortion can cop mildly crunchy tones to that of serious EL34 territory. It delivers crunch in spades!

Oh please check out Juan & Cleggy's awesome webpage here!

<http://stompage.juansolo.co.uk/>

Feature Set:

- Built-in Charge pump for 18v operation
- Pads line up with rullywow.com 3PDT boards
- Easy jumper for use with many different charge pumps
- Very easy to build!


Bill of Materials:

Caps			Resistors			Pots	
C1	100n	film	R1	2M2		TONE	50kB
C2	47p	ceramic	R2	10k		VOL	500kB
C3	100n	film	R3	33k		GAIN	1MB
C4	470pF	ceramic	R4	1k			
C5	220n	film	R5	47k			
C6	3n3	film	R6	10k			
C7	10uF	electro	IC			Diodes	
C9	10uF	electro	IC1	4558		LED1	3MM RED
C10	100uF	electro	IC2	TC1044*		LED2	3MM RED
C11	100n	film				Z1	1N4739

Build Tips:


- For the easiest build experience, try using Rullywow 3PDT breakout boards available [here](#). They make wiring the stomp switch a breeze!
- You can use other charge pump ICs besides the TC1044. Common CPs are: ICL7660, MAX1044, TC1044, and LT1054.
- Don't forget the solder jumper (J3) under the IC2, which is the charge pump. You will want to put a drop of solder across this before soldering in your chip or socket if your charge pump requires connecting pins 1 and 8. Most require connecting these pins **except the LT1054. If you fail to connect the jumper and your CP requires it...you will most likely hear an audible 'whine' from the circuit.**
- It is a good idea to solder components from shortest height to tallest. In this case, you should start with resistors, diodes, film caps, electrolytic caps, and IC/sockets.
- Before putting your creation into its enclosure, you should always test it! If it doesn't work outside the enclosure, it won't work inside (I promise!)

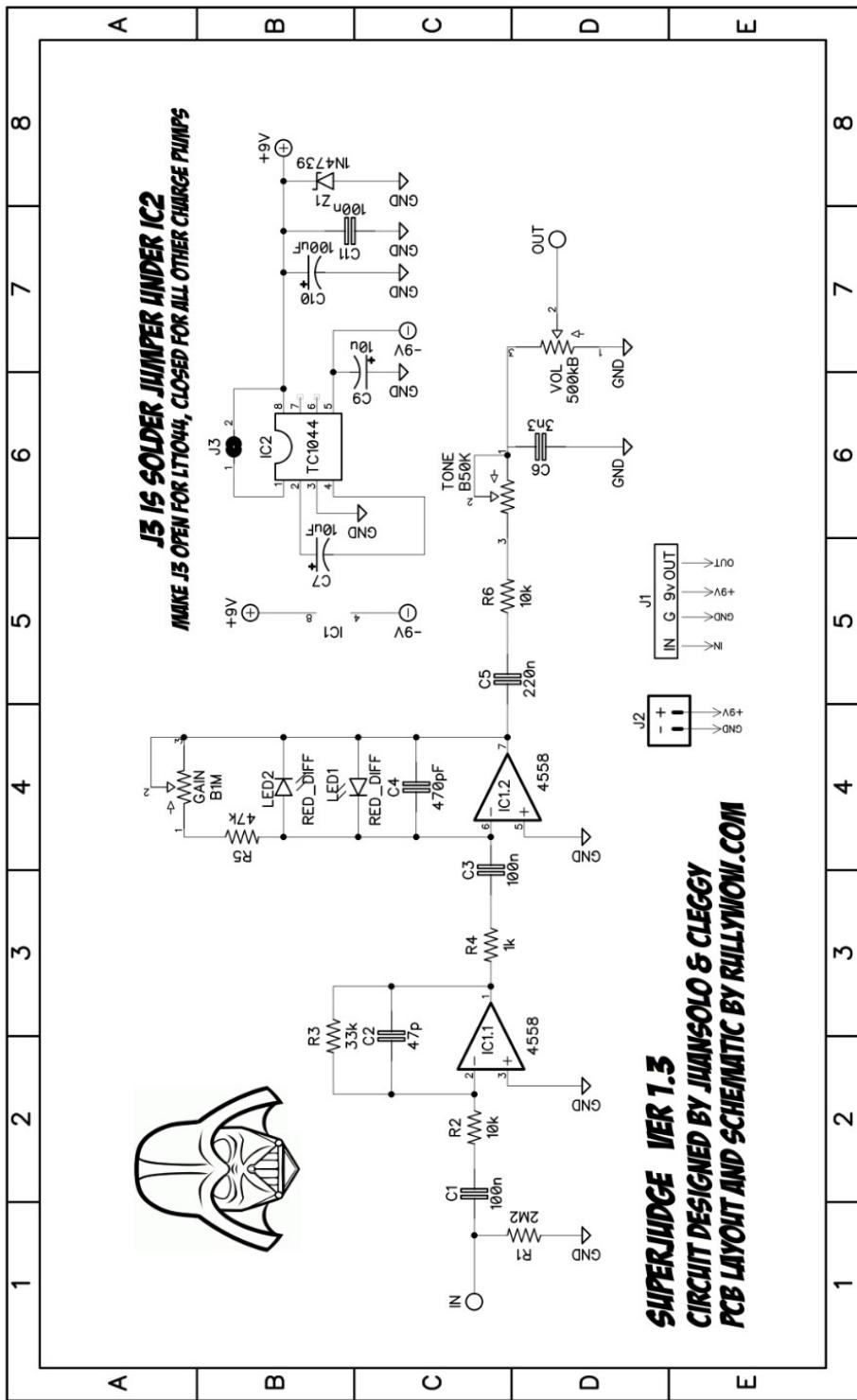- The LEDs (used for clipping) are suggested to be 3mm red diffused. You may want to socket these and try different types of diodes. You could use anything from green leds, to 1n4148, etc. Red seems to have the most “EL34 type” crunch.
- **Make sure you use capacitors rated at least 25v.** Since the circuit increases the 9v to 18v, you want to be sure all your components can handle it.



Drill Guide (1590B) :

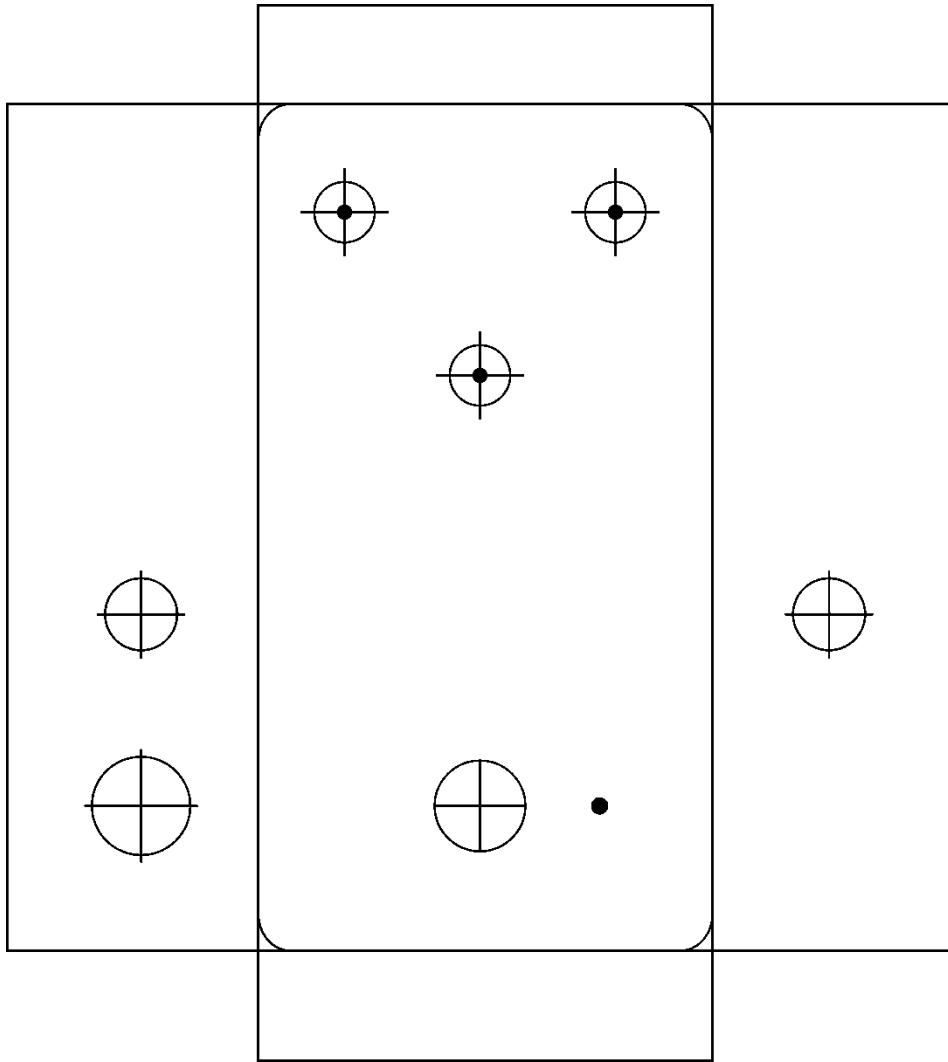This is an **APPROXIMATE** drill guide. Enclosures differ in size so be sure to measure before your commit to drill!



Terms of Use:

- PCBs from www.rullywow.com are intended for DIY use and are not allowed for commercial resale. It is OK to build (and sell) a few pedals for your friends, bandmates, yourself (that is what the DIY guitar pedal community is all about!). Special thanks to Juan and Cleggy for letting this become a PCB available to the DIY community!